

2013

(November)

PHYSICS

(Major)

Course : 504

(Electronics)

Full Marks : 60

Pass Marks : 24

Time : 3 hours

*The figures in the margin indicate full marks
for the questions*

1. Answer as directed :

1×6=6

(a) The peak voltage in the output of a half-wave rectifier without filter is 10 V. The d.c. component of output voltage is

(i) $\frac{10}{\sqrt{2}}$ V

(ii) $\frac{10}{\pi}$ V

(iii) 10 V

(iv) $\frac{20}{\pi}$ V

(Choose the correct answer)

(2)

(b) The unit of the ratio of mobility and diffusion coefficient of a semiconductor is

- (i) V^{-1}
- (ii) cmV^{-1}
- (iii) $V cm^{-1}$
- (iv) Vs

(Choose the correct answer)

(c) The voltage gain of an amplifier with 9% negative feedback is 10. The voltage gain without feedback will be

- (i) 90
- (ii) 10
- (iii) 100
- (iv) 1.25

(Choose the correct answer)

(d) The maximum theoretical efficiency of a class B push-pull transistor amplifier is

- (i) 25%
- (ii) 50%
- (iii) 70.7%
- (iv) 78.5%

(Choose the correct answer)

(e) An oscillator using series resonant circuit with inductor L and capacitor C produces oscillations of frequency f . If L is doubled and C is changed to $4C$, the frequency of oscillation will be

(i) $f/2$

(ii) $f/4$

(iii) $8f$

(iv) $f/2\sqrt{2}$

(Choose the correct answer)

(f) What is the minimum number of gates required to perform the logic operation $A + \overline{AB}$?

2. Answer the following :

$2 \times 6 = 12$

(a) Distinguish between Zener breakdown and avalanche breakdown in a $p-n$ junction.

(b) Find the ratio of electron to hole concentration in an n -type silicon crystal having donor concentration $1.4 \times 10^{24} \text{ m}^{-3}$ and intrinsic carrier concentration $1.4 \times 10^{18} \text{ m}^{-3}$.

(c) The power gain of a $C-B$ amplifier is 800 and the voltage amplification factor is 840. Find the collector current, when the base current is 1.2 mA.

- (d) The capacitor used in a Wien bridge oscillator is of 300 pF. What should be the value of the resistance so that the frequency of oscillation is 20 Hz?
- (e) What is negative feedback? How can it increase the stability of an amplifier?
- (f) Using Boolean algebra, prove that

$$(A + B)(A + C) = A + BC$$

3. Distinguish between metal, semiconductor and insulator in terms of energy bands. Define Fermi level of a material and indicate its position for *p*-type and *n*-type semiconductors. Show that the Fermi level for an intrinsic semiconductor lies in the middle of the forbidden gap. 3+2+3=8

Or

Explain the formation of potential barrier in a *p-n* junction. Derive an expression for the barrier potential. What happens to the barrier under forward and reverse biased conditions? 3+4+1=8

4. What is ripple factor? Calculate the ripple factor of a full-wave rectifier. Discuss any one method for minimizing ripple factor. 1+3+2=6

5. (a) Explain how amplification is achieved in a transistor. 3

(b) What is transistor biasing? Discuss the voltage divider bias method of transistor biasing and calculate the stability factor.

$$1+(3+2)=6$$

Or

Draw the circuit diagram of a R-C coupled amplifier and give its low-frequency equivalent circuit. Calculate the gain at low-frequency range and explain why gain increases with frequency.

$$2+4=6$$

6. (a) Draw the electrical equivalent circuit of a vibrating piezoelectric crystal. Find the expressions for resonant frequencies in the two modes of vibrations and show that they are approximately equal.

$$1+(3+1)=5$$

(b) What is the function of silicon dioxide layer in an IC? How is it formed? 2

(c) Show how an OP-AMP can be used as a differentiator or an integrator. 2

7. (a) Draw the logic diagram of a full-adder and discuss its working by giving the truth table. 4

(6)

- (b) State De Morgan's theorem and apply it to show that

$$\overline{\overline{A+B+C}} = (A+B)C \quad 2+2=4$$

- (c) What is a Karnaugh map? How many squares are there in a three-variable Karnaugh map? 1+1=2
